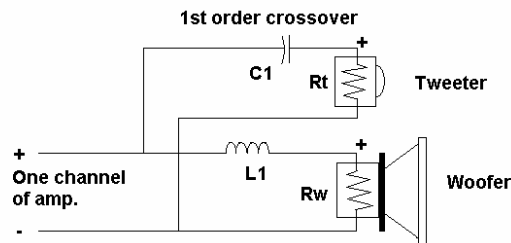


## Speaker Crossover

### 1<sup>st</sup> Order Crossover – 2 Way Speakers

$$C = \frac{1}{6.28318 F_c R_t} = \frac{.159155}{F_c R_t}$$

Where  $F_c$  = Crossover Frequency (Hz)  
 $R_t$  = Tweeter rated impedance ( $\Omega$ )



### 2<sup>nd</sup> Order Crossover – 2 Way Speakers


Tweeter Section

Woofer Section

$$C_1 = \frac{1}{4\pi F_c R_t}$$

$$C_2 = \frac{1}{4\pi F_c R_w}$$

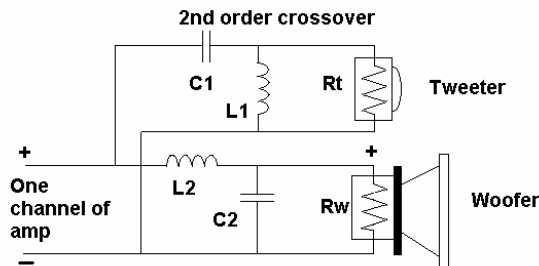Where  $C_1, C_2$  = Tweeter Section Capacitance ( $\mu\text{F}$ )  
 $R_t$  = Tweeter rated impedance ( $\Omega$ )  
 $R_w$  = Woofer rated impedance ( $\Omega$ )  
 $F_c$  = Crossover Frequency (Hz)



### 3<sup>rd</sup> Order Crossover – 2 Way Speakers


Tweeter Section

Woofer Section

$$C_1 = \frac{106,103}{4\pi F_c R_t}$$

$$C_3 = \frac{272,207}{4\pi F_c R_w}$$

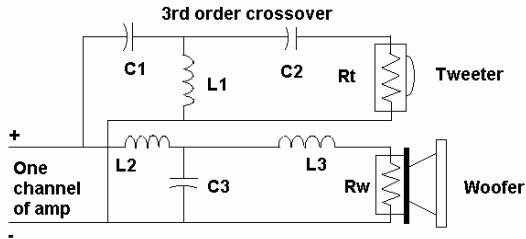Where  $C_1, C_2$  = Tweeter Section Capacitance ( $\mu\text{F}$ )  
 $C_3$  = Tweeter Section Capacitance ( $\mu\text{F}$ )  
 $R_t$  = Tweeter rated impedance ( $\Omega$ )  
 $R_w$  = Woofer rated impedance ( $\Omega$ )  
 $F_c$  = Crossover Frequency (Hz)



### 1<sup>ST</sup> Order Crossover – 3 Way Speakers

Tweeter Section  
 (High Pass)

Woofers Section  
 (Band Pass)

$$C_1 = \frac{159,155}{F_{HC} R_t}$$

$$C_2 = \frac{159,155}{F_{LC} R_m}$$

Where  $C_1$  = Tweeter Section Capacitance (uF)  
 $C_2$  = Mid-range Section Capacitance (uF)  
 $F_{HC}$  = High frequency Crossover Frequency (Hz)  
 $F_{LC}$  = Low frequency Crossover frequency (Hz)

1st order 3 way speaker crossover

